
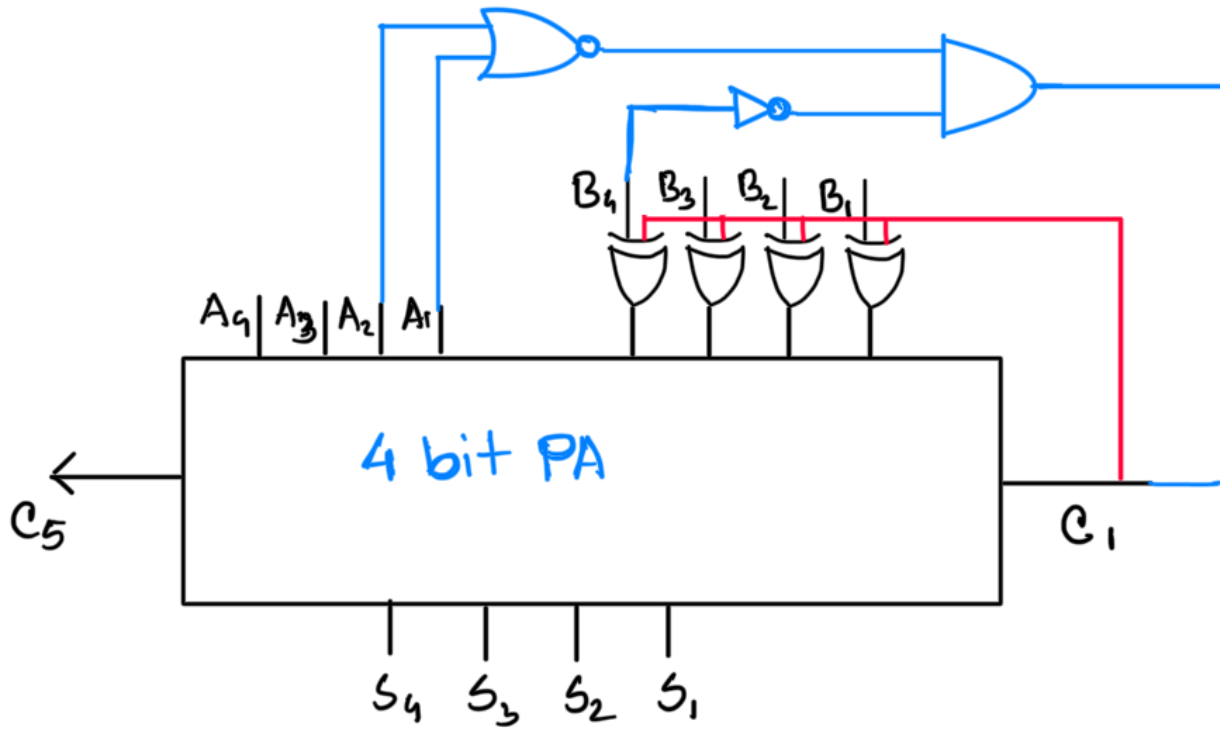


Quiz - 3

i

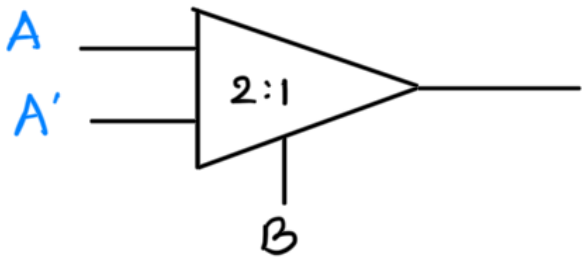


ii) XOR using 2:1 mux



A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

	1 ₀	1 ₁
A'	0	1
A	1	0
	A	A'

iii) XNOR using 2:1 mux

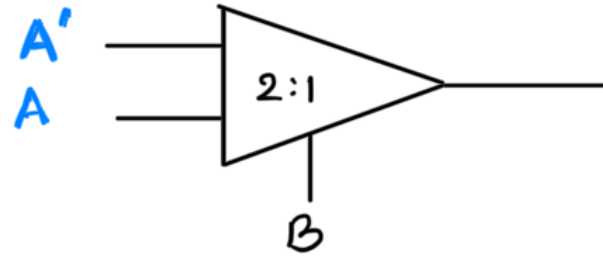

A	B	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

	1 ₀	1 ₁
A'	1	0
A	0	1
	A'	A

iii

1 ₃	1 ₂	1 ₁	1 ₀	A ₁	A ₀
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	0	0

A₁

1 ₃ 1 ₂ \ 1 ₁ 1 ₀	00	01	11	10
00	X			
01	1	1		1
11	1	1		1
10	1	1		1

$$= 1_2 1_1' + 1_3 1_1' + 1_2 1_0' + 1_3 1_0'$$

A₀

1 ₃ 1 ₂ \ 1 ₁ 1 ₀	00	01	11	10
00	X		1	1
01			1	
11	1			
10	1	1	1	1

$$= l_3 l_2' + l_2' l_1 + l_3 l_1' l_0' + l_3' l_1 l_0$$